

# ATU and wifi connectivity for the MkII SARC WSPR TX

G0CJG

1 October 2021

Presentation to the Shirehampton Amateur Radio Club

# Background

- Mk II WSPR TX was designed by G3YHV (HW and SW) + SW contributions from G0CJG
- It is, standalone, a capable unit and doesn't need more than an antenna and a power supply for hours of fun
- It is also a nice platform for tinkerers/hackers. G3YHV has chosen a capable PIC chip. There are plenty of unused IO pins and coding space.
- None of the ideas to be presented are "kit ready" but they have all been breadboarded to show basic feasibility
- I'd like to acknowledge ATU code and ESP8266 code shared by Steve, W8TTY. See last slide for details


# Breadboarded Functions

- Dedicated ATU for the WSPR box
- Set clock from the internet over wifi
- Am I getting out? display latest reports from [wsprnet.org](http://wsprnet.org) using wifi
- Antenna Switch
- DC to DC converter (from 10-40V to 7V )

# SARC WSPR box ATU requirements

- Only needs to tune for 10 fixed frequencies (1.8-28MHz)
- PA only 100mW class A
  - power reflected from the load won't kill it.
  - ATUs designed for 150W generally won't tune on 100mW
- Must be fully integrated with WSPR box.
  - Once set up for a particular Antenna it should be automatic

# ATU100 (kit widely available)

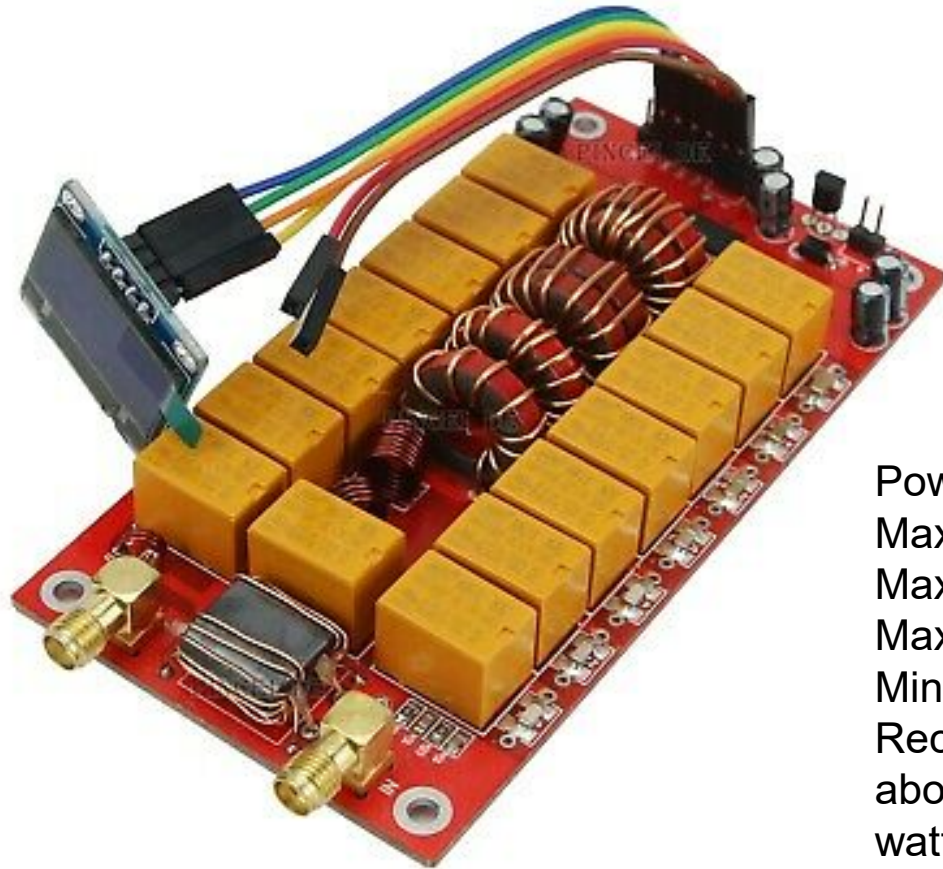

Power supply range: 10 - 15 VDC

Max current : 450mA

Max working power: 100 watts

Max measured power: 150 watts

Minimum power for tuning start: 1 watt

Recommended maximum power while tuning not above 30 watts. (after tuning you can set 100 watts and work on this power)

Maximum inductance set: 8.5  $\mu$ H

Minimal step for setting inductance: 0.1  $\mu$ H


Maximum installed capacity: 1870 pF

Minimal step for setting capacity: 10 pF


Uses 7 capacitors and 7 coils

based on PIC 16F1938.

# ATU100

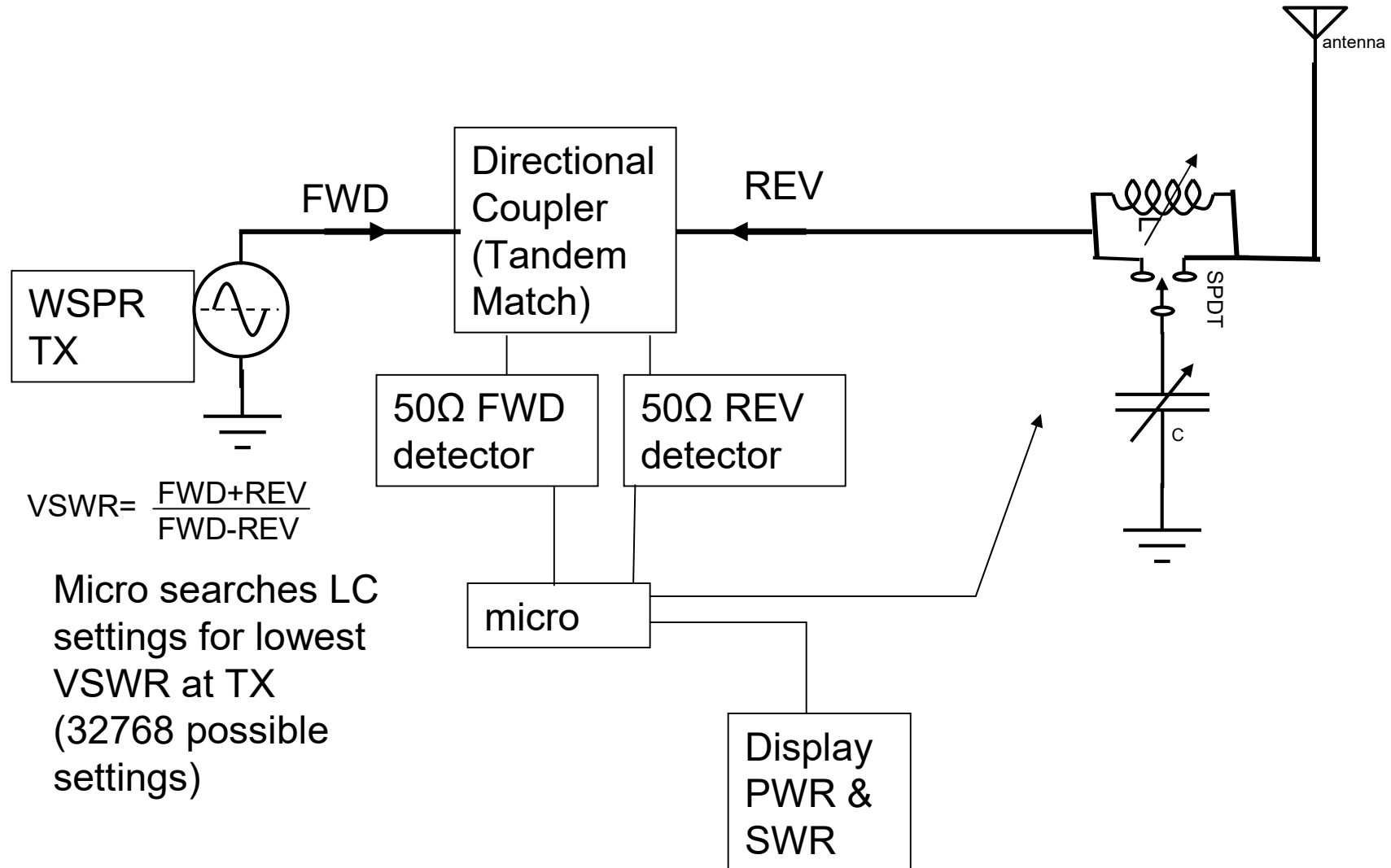
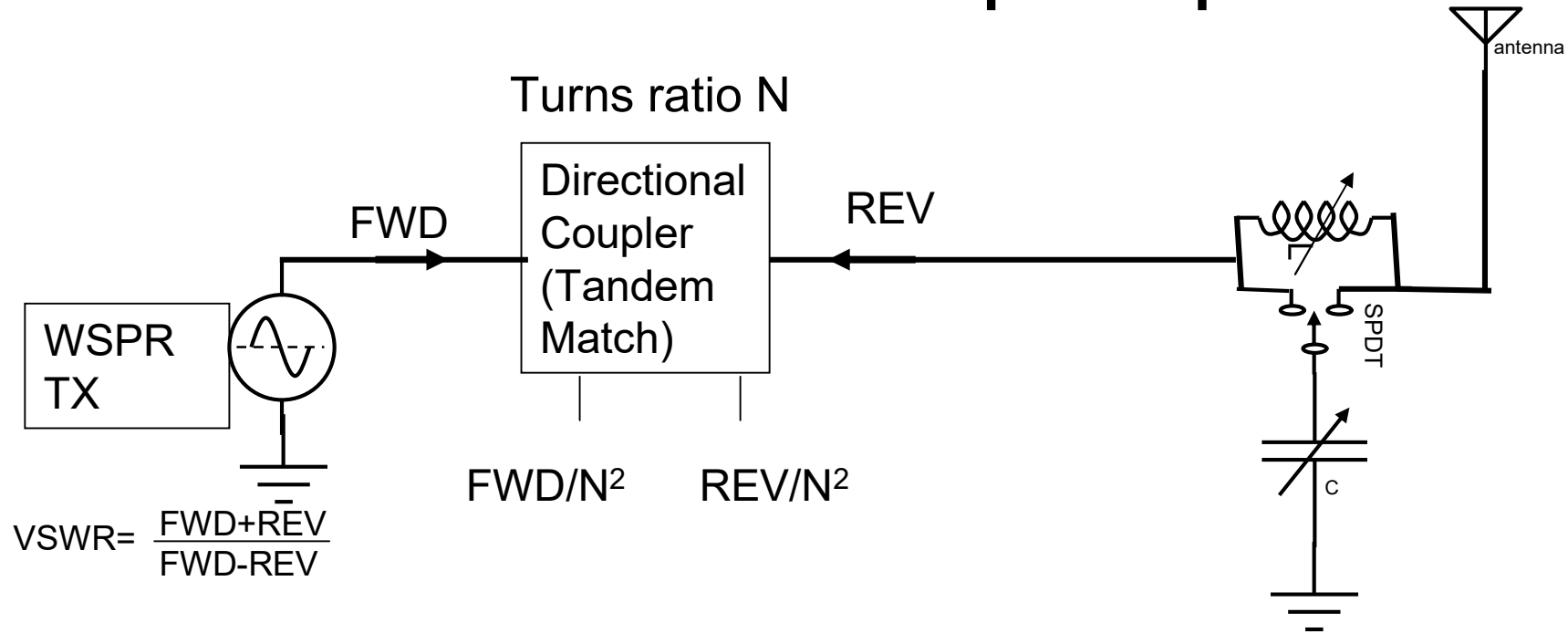
# ATU100 Effect of Tandem Match turns ratio on coupled power




ATU100 documentation recommends changing N from 10 to 5 to reduce needed tune power from 5W to 1W

With this approach To tune on 100mW would require N= 1.414

This would unfortunately dissipate half the forward power in the forward detector

# ATU100 out of the box

Why does QRP tuning fail? Some clues....

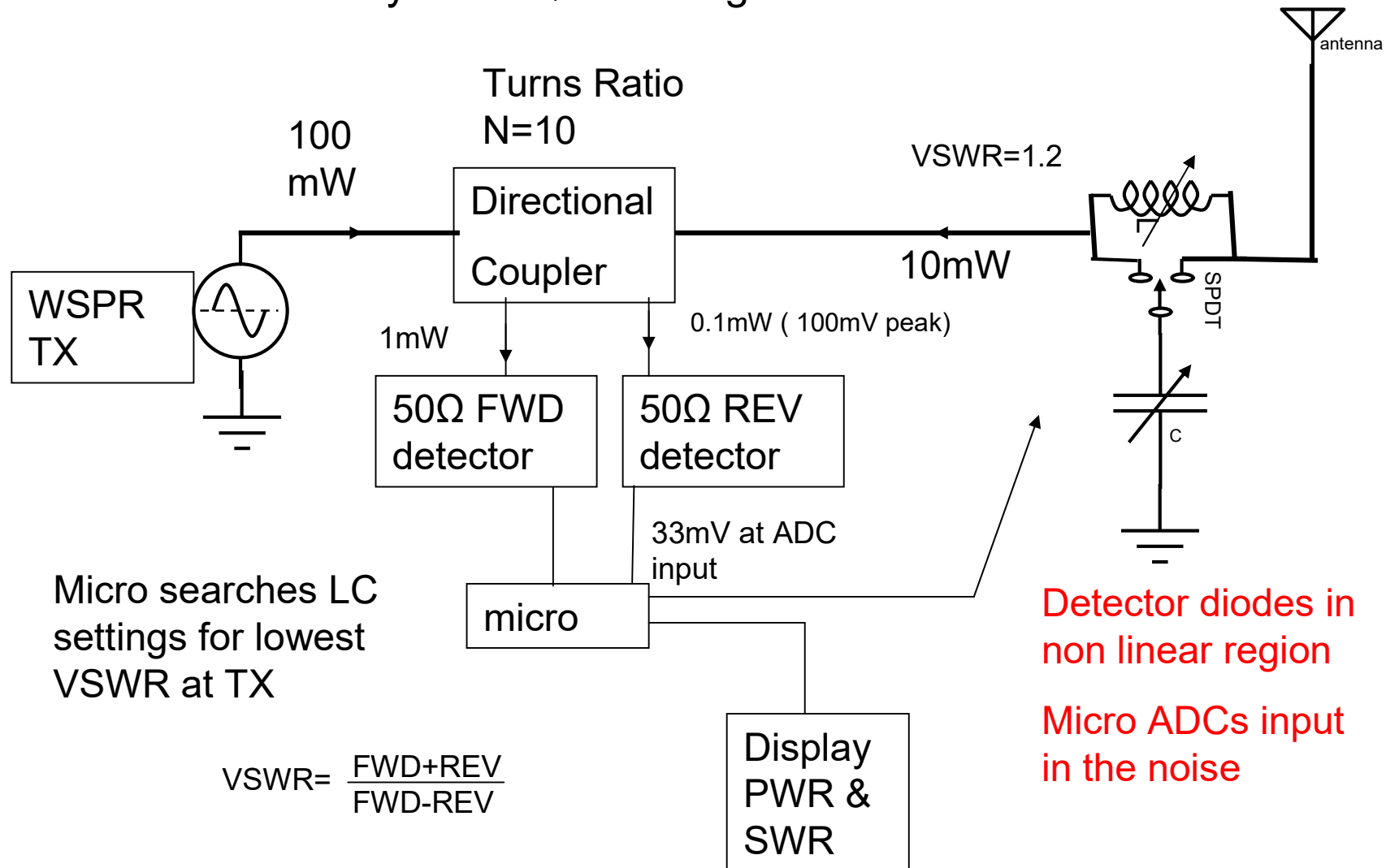



# QRP tuning solutions

1. Change the detectors from half wave to full wave and add some DC gain before the micro ADC
2. Use an offline resistive bridge detector (as in the MFJ269 SWR meter )
3. Dump the tandem match and maximize antenna current rather than reduce VSWR

Approach 1 & 2 require an extra PCB whereas 3 only requires a few changes on the ATU100 board


## Approach 3

Minimizing the reflected power is important for a 100W solid state class AB amp  
But not so important for a 100mW class A amp. So dump the Tandem Match.

Maximizing the antenna current compensates for frequency related change in the output impedance of the PA as well as antenna impedance changes


The current detector with an input impedance of 1000 Ohm should dissipate 10% of the input power and put about 3V across the detector diode.

# ATU100 QRP current sensor detail

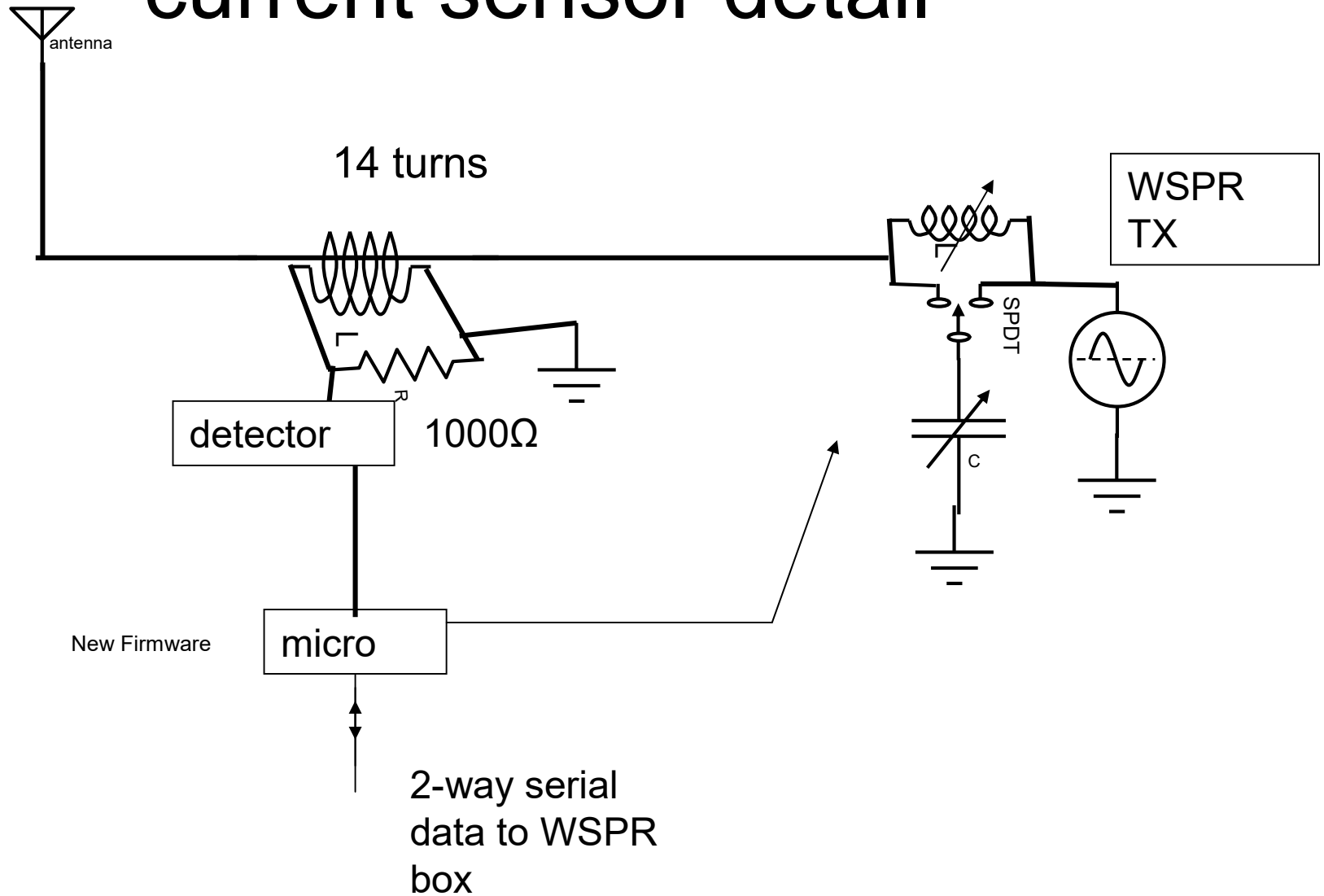


# ATU100 mods for current sensor


Modified

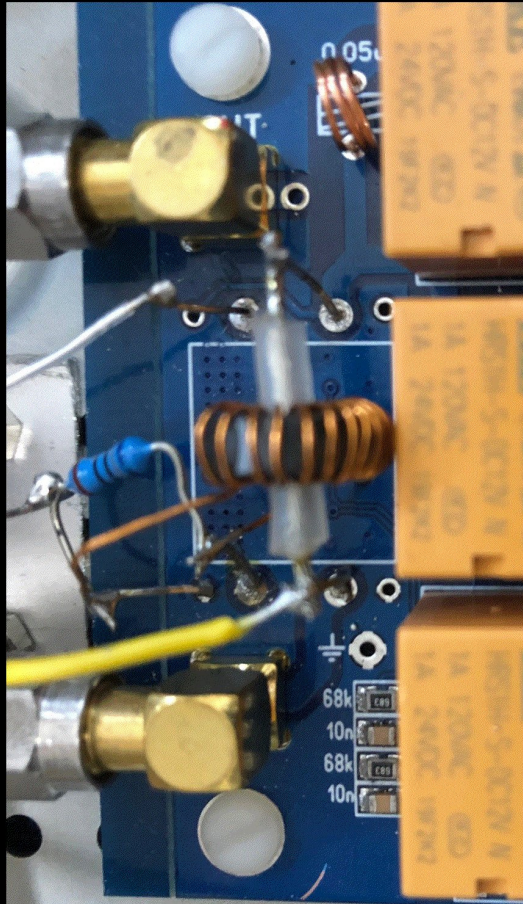

Original

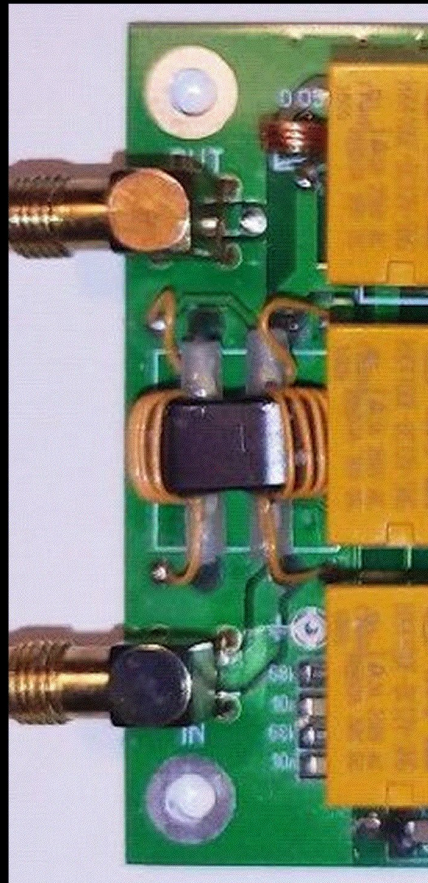


Remove  
Resistor

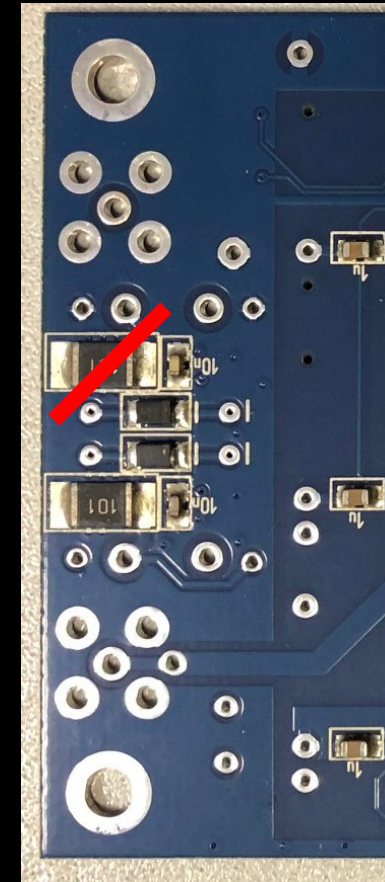
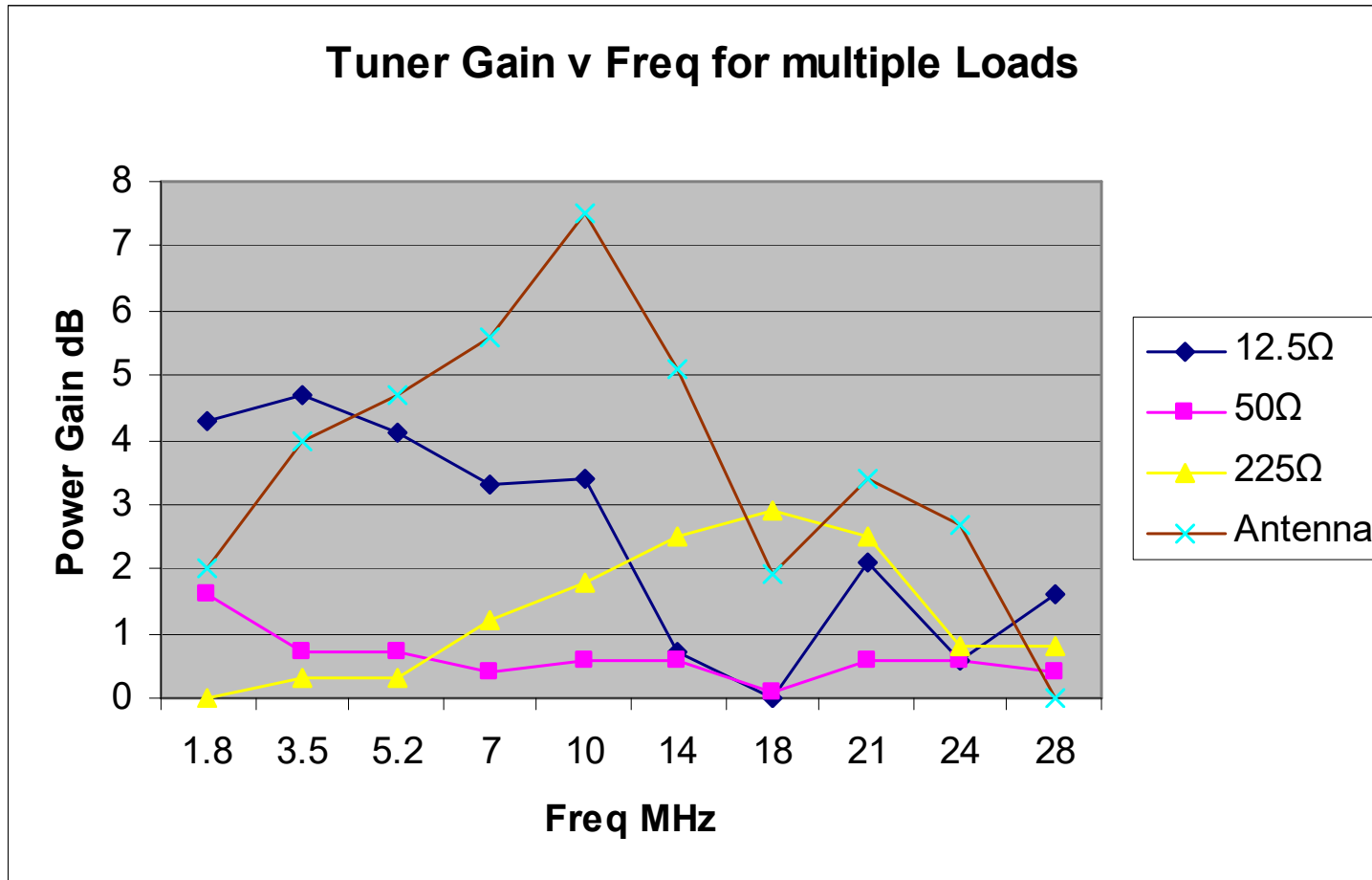
# Performance of current sensor ATU

The tuner gain with the antenna load is the significant result



Antenna is a 30m Doublet

# ATU100 integration with the SARC WSPR TX

- The ATU tuning is done during WSPR SETUP only. It takes a couple of minutes. The optimum values for each band with the selected antenna are stored in the ATU
- In normal WSPR operation on each band change the ATU is automatically commanded to retrieve and set the stored value.
- The WSPR TX uses slow speed serial data at logic levels to send commands to the ATU100 and to read data returned.
- The ATU100 firmware was written in Proton Basic.

# Wifi connectivity for the WSPR box

Wifi interface and processor  
for about £5-10

Nodemcu Esp8266

Code written  
using Arduino  
environment



Lots of pins – but  
only use 4, vcc,  
gnd, serial in and  
serial out

# WSPR time

## combine NTP over wifi and RTC

- NTP network time protocol
- RTC realtime clock
- If NTP service available the RTC is set on every power-up or every 24 hours during continuous operation
- Don't need to use the house wifi, you can use the hotspot on your phone

# Am I getting out?

- We generally use [wsprnet.org](http://wsprnet.org) in a browser or one of the phone apps (eg [wspr watch](#))
- However would be nice to get an immediate readout from the WSPR box itself
- Using the ESP8266 wifi connection the box retrieves WSPRNET reports after each TX.
- Displays number of reports and distance of furthest report.



# W8TTY acknowledgement

- Steve, W8TTY, kindly shared his experimental ATU100 C++ project code that works under the MPE (free) development platform from which I learned a lot.
- I subsequently used the Proton basic environment for my ATU code because I was more familiar with it.
- Steve also shared details of his use of the ESP8266 to control an ATU which inspired me to pursue wifi connectivity for the WSPR box